



Week 7 Review

Question #1

- What is the result of the following operation?

$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline \end{array}$$



$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline 0000 \\ 1101 \\ 0000 \\ 1101 \\ \hline 1000010 \end{array}$$

Verify!


→ 10

→ 13

→ 130

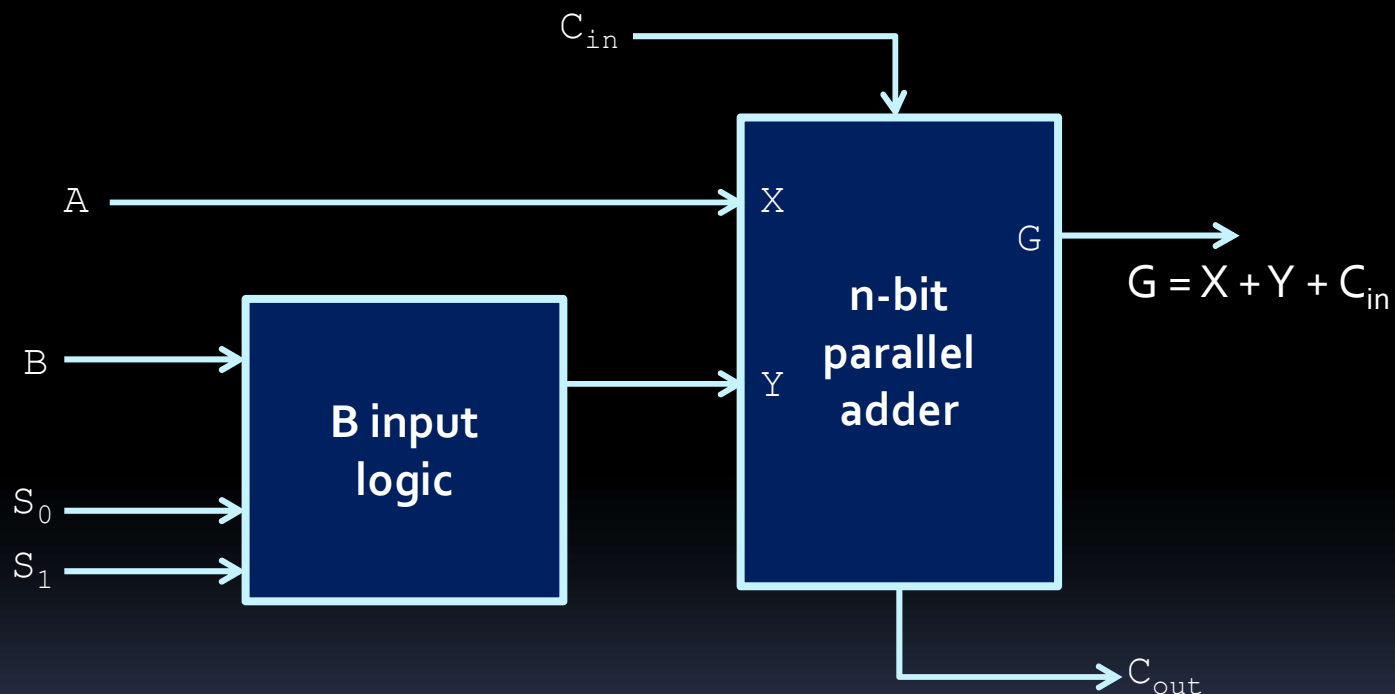Question #2

- The arithmetic unit of the ALU looks like this:




- What values for S₀, S₁ and C_{in} do we need in order to subtract B from A?

Question #2 (cont'd)

- Kind of an unfair question, in that there's a table that fills in some necessary details:

Select		Input	Operation	
S_1	S_0	Y	$C_{in}=0$	$C_{in}=1$
0	0	All 0s	$G = A$ (transfer)	$G = A+1$ (increment)
0	1	B	$G = A+B$ (add)	$G = A+B+1$
1	0	\bar{B}	$G = A+\bar{B}$	$G = A+\bar{B}+1$ (subtract)
1	1	All 1s	$G = A-1$ (decrement)	$G = A$ (transfer)

Question #2 (cont'd)

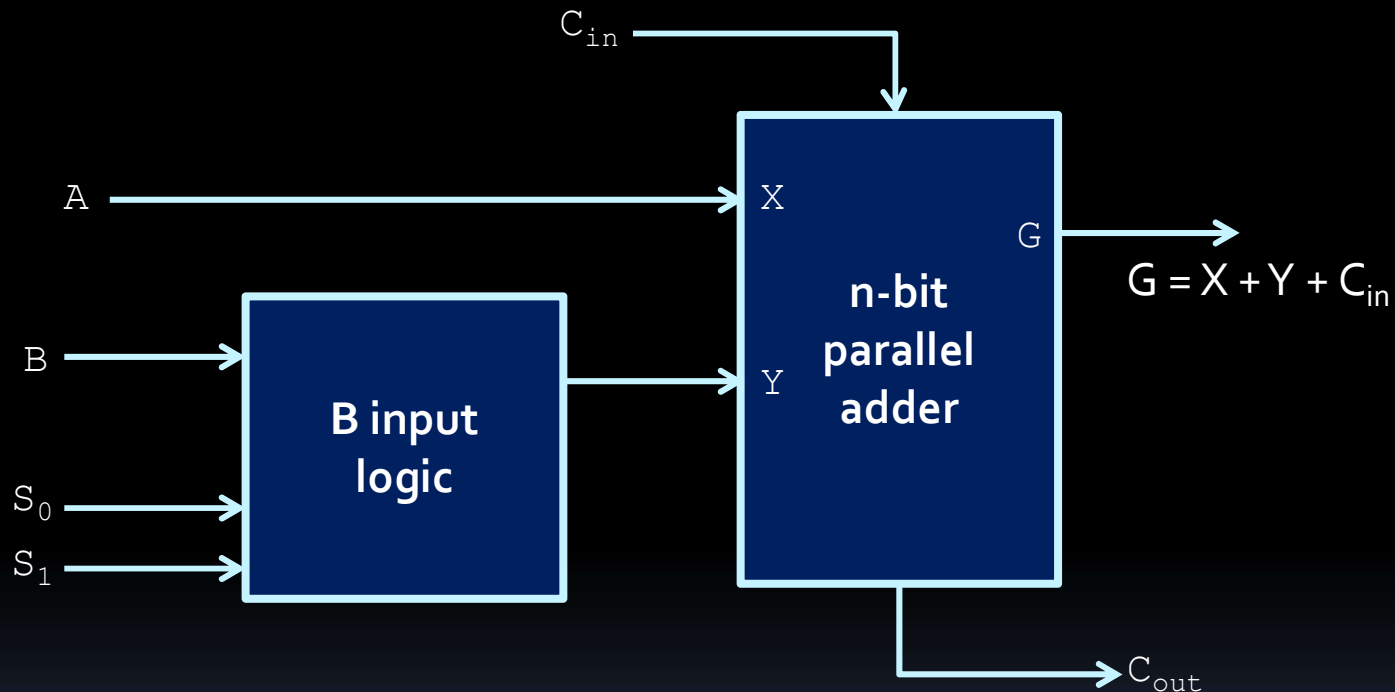

- To subtract B from A , you must set $S_0=0$, $S_1=1$ and $C_{in}=1$.

Question #3

- In an ALU, S_0 and S_1 determine which kind of arithmetic or logical function to perform. But there are 3 select signals that go into the ALU.

What does S_2 do?

Question #3 (cont'd)

